



CPCS 211: Digital Logic Design

Chapter 5 : Designing Compinational Systems
Part II (5.4 – 5.6 & 5.8)

Outline

- Multiplexers
- DeMultiplexers
- Three State Gates and Bus
- Gate Arrays: ROMs, PLAs and PALs
- Designing with Read Only Memories
- Larger Examples of Combinational Circuits

Multiplexer

- A multiplexer, often referred as a **mux**, is basically a switch that passes one of its data inputs through to the output, as a function of a set of select inputs
- A multiplexer is a combinational circuit that selects binary information from one of many input lines and directs it to a single output line


Multiplexer

- Selection of a particular input line is controlled by a set of selection lines
- Normally there are 2^n input lines and n selection lines whose bit combinations determine which input is selected
- A two-to-one line multiplexer connects one of two 1-bit sources to a common destination, as shown next

Multiplexer

A two-way multiplexer and its logic symbol are shown

Figure 5.11 Two-way multiplexer.

 




S	out
0	w
1	x

Four-Way Multiplexer

- A four-to-one line multiplexer is shown in Figure 5-12a
- Each of the four inputs is applied to one input of AND gate
- Selection lines S_1 and S_0 are decoded to select a particular AND gate
- Outputs of the AND gates are applied to a single OR gate that provides the one-line output
- A multiplexer is also called a **data selector**
- – since it selects one of many inputs and steers the binary information to the output line

Four-Way Multiplexer


Figure 5.12 (a) A four-way multiplexer. (b) From two-way multiplexers. (c) Logic symbol.

   

S_1	S_0	out
0	0	w
0	1	x
1	0	y
1	1	z

Four-Way Multiplexer

 - Output equals input
 - w if select inputs (S_1, S_2) are 00
 - x if they are 01
 - y if they are 10
 - z if they are 11
- Circuit is very similar to that of decoder, with one AND gate for each select input combination
- Some multiplexers also have *enable* inputs, such that *out* is 0 unless the enable is *active*




(c)

S_1	S_0	<i>out</i>
0	0	w
0	1	x
1	0	y
1	1	z

Multibit Multiplexer


- If inputs consist of set of 16-bit numbers, and control inputs choose which of these numbers is to be passed on, then we would need 16 multiplexers, one for each bit
- We could build 16 of the circuits of Figure 5.12a, utilizing 64 three-input AND gates and 16 four-input OR gates
- Alternative is to use one decoder to drive all the multiplexers
- First 3 bits of such circuit are shown in Figure 5.13

Figure 5.13 A multibit multiplexer.

 

Multibit Multiplexer Operation

 
- If $S_0 = 0$, $S_1 = 0$, *decoder active output* = 0
 - $out0 = w_0$
 - $out1 = w_1$
 - $out2 = w_2$



Multibit Multiplexer Operation

If $S_0 = 0$, $S_1 = 1$, decoder active output = 1

 
- $out0 = x_0$
- $out1 = x_1$
- $out2 = x_2$



Multibit Multiplexer Operation

If $S_0 = 1$, $S_1 = 0$, decoder active output = 2

 
- $out_0 = y_0$
- $out_1 = y_1$
- $out_2 = y_2$



Multibit Multiplexer Operation

If $S_0 = 1$, $S_1 = 1$, decoder active output = 3

 
- $out0 = z_0$
- $out1 = z_1$
- $out2 = z_2$



Example

- Consider the Boolean function: $f(a, b, c) = \sum (0, 1, 2, 5)$. TT is as shown.
- It can be implemented with eight-way multiplexer, with values of f as input to MUX and variables a , b and c as control inputs (i.e. select lines)
- This MUX is shown as follows:

a	b	c	f
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

 


Example cont.

- Same Boolean function can also be implemented with four-way mux
- To do this, we would rewrite truth table as follows; this leads to the shown implementation

a	b	c	f
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

a	b	f		f
		$c = 0$	$c = 1$	
0	0	1	1	1
0	1	1	0	c'
1	0	0	1	c
1	1	0	0	0

 


Commercial Multiplexers

- 74151

- 1-bit eight-way mux with one active low enable input, EN' , and both an uncomplemented (active high) and a complemented (active low) output

 
- Inputs are labeled $A7$ to $A0$ (corresponding to the binary select)
- Outputs are Y and Y'
- Select inputs are labeled $S2$, $S1$, and $S0$, in that order



Commercial Multiplexers


- 74153

- Contains 2 (dual) four-way multiplexers, *A* and *B*, each with its own active low enable (*ENA'* and *ENB'*)
 - Inputs to first are labeled *A3* to *A0* and its output is *YA*
 - Inputs to second are *B3* to *B0*, with output *YB*
 - Two select lines (labeled *S1* and *S0*)
 - Same select signal is used for both multiplexers
 - This would provide 2 bits of multiplexer for choosing among four input words

 

Commercial Multiplexers

 
- 74157
 - Contains 4 (quad) two-way multiplexers, with a common active low enable EN' and a single common select input S ; multiplexers are labeled A , B , C , D
 - Inputs $A0$ and $A1$
 - Output YA for the first multiplexer
 - This provides 4 bits of a two-way selection system



DeMultiplexer


- Demultiplexer (**demux**) is inverse of mux
 - It routes signal from one place to one of many
 - It is circuit that receives information from single line and directs it to one of 2^n possible outputs
 - Selection of specific output is controlled by bit combination of n selection lines
- Figure shows one bit of four-way **demux**, where **a** and **b** select which way signal, **in**, is directed
 - Circuit is same as for four-way decoder with signal **in** replacing **EN**

Figure 5.14 A four-way demux.

 


DeMultiplexer Operations

 If $a = 0$, $b = 0$, in input is directed to out_0




DeMultiplexer Operations

 If $a = 0$, $b = 1$, in input is directed to out_1




DeMultiplexer Operations

 If $a = 1$, $b = 0$, in input is directed to out_2



DeMultiplexer Operations

 If $a = 1$, $b = 1$, in input is directed to out_3




Three State Gates

- Some design techniques allow us to connect outputs of two gates to each other
- More commonly used is referred to as **three-state** (or **tristate**) output gates

Three State Gates

- In a three-state gate, there is enable EN input, shown on side of gate
 - If EN is **active** (active high or active low), gate behaves as usual
 - If EN is **inactive**, output behaves as if it is not connected (open circuit)
 - Output represented by Z
- TT and circuit representation of a three-state buffer (with active high enable) is shown


Figure 5.15 A three-state buffer.

 

Three State Gates

- Three-state buffers with active low enables and/or act as a three-state NOT gate
- With three-state gates, we can build a multiplexer without the OR gate
- e.g., circuit of Figure 5.16 is two-way mux
 - EN is control input, determining whether
 - $f = a$ (when $EN = 0$)
 - $f = b$ (when $EN = 1$)
- Often used for signals that travel between systems

Figure 5.16 A multiplexer using three-state gates.

 

EN	f
0	a
1	b


Bus

- A *bus* is a set of lines over which data are transferred
- Sometimes, that data may travel in either direction between devices located physically at a distance
- Bus itself is really just a set of multiplexers, one for each bit in the set


Example

The following circuits show a bit of two implementations of bus using

- AND and OR gates
- three-state gates

 

(a) Using AND/OR Gates

 


(b) Using Three-State Gates

 
Example cont.

Major difference is

- the **two** long wires per bit between the systems for AND-OR multiplexer compared to only **one** for the three-state version



(a) Using AND/OR Gates

 

(b) Using Three-State Gates


Example cont.

- Difference is even greater if what is being transferred between systems is 32-bit words; in that case, there would be 32 multiplexers
 - AND–OR system would require 64 wires between systems, whereas
 - three-state version would require only 32
- Further, if the **enable** signal came from one of the systems (instead of being generated internally in each), that would only add one wire, no matter how long the words are

Gate Arrays

- Gate arrays are also called *Programmable Logic Devices* (PLDs)
- Gate arrays are one approach to the rapid **implementation** of fairly complex systems
- They come in several varieties, but all have much in common
- Basic concept is illustrated in Figure 5.17 for system with 3 inputs and 3 outputs where **dashed lines indicate possible connections**
- These devices **implement SOP** expressions


Figure 5.17 Structure of a gate array.

 

Gate Arrays

- In this case, three functions of three variables can be implemented
- However, since there are only 6 AND gates
 - – a maximum of 6 different product terms can be used for the three functions
- Array only requires uncomplemented inputs

Figure 5.17 Structure of a gate array.

 

Example


- Consider the following three functions:

$$f = a'b' + abc$$

$$g = a'b'c' + ab + bc$$


$$h = a'b' + c$$

 - These functions can be implemented using the shown gate array
- In this implementation, the solid lines show the actual connections



 Example cont.

- Previous version of the diagram is rather cumbersome, particularly as the number of inputs and the number of gates increase
- Thus, rather than showing all of the wires, only a single input line is usually shown for each gate, with X's or dots shown at the intersection where a connection is made
- Previous circuit can be redrawn as shown



Types of Combinational Logic Arrays

Three common types of combinational logic arrays

– **Programmable Logic Array (PLA)** - the most general type

- User specifies all connections (in both AND array and OR array)
- Can create any set of SOP expressions (and share common terms)


– **Read-Only Memory (ROM)**

- AND array is fixed
- It is just a decoder, consisting of 2^n AND gates for an n -input ROM
- User only specify connections to OR gate; thus, it produces sum of minterms solution


– **Programmable Array Logic (PAL)**

- Connections to the OR gates are specified
- User can determine the AND gate inputs
- Each product term can be used only for one of the sums


Types of Combinational Logic Arrays

 

PLA

 

ROM

 


PAL

Types of Combinational Logic Arrays

- In addition to the shown logic, many programmable devices make the output available in either *active high* or *active low* form
 - Active low means complement of output, that is, f' instead of f
 - This just requires an XOR gate on the output with the ability to program one of the inputs to 0 for f and to 1 for f'
 - Output logic for such case is shown


Figure 5.18 A programmable output circuit.

 

Types of Combinational Logic Arrays


- Some programmable devices have three-state buffer at output, which may be enabled either by an enable input line or one of logic AND gates
 - Allows output to be easily connected to a bus
- Sometimes, output is fed-back as another input to the AND array
 - Allows for more than two-level logic (most commonly in PALs)
 - Also allows that output to be used as input instead of output, if three-state output gate is added, as shown

Figure 5.19 Three-state output.

 

Designing with ROMs

 - To design a system using a ROM, function should be represented in minterms
- ROM has one AND gate for each minterm
 - Connect the appropriate minterm gates to each output
- This is really the same type of circuitry as the decoder implementation of a sum of product expression



Example

Implement the following three functions with ROM

$$W(A, B, C, D) = \Sigma m(3, 7, 8, 9, 11, 15)$$


$$X(A, B, C, D) = \Sigma m(3, 4, 5, 7, 10, 14, 15)$$

$$Y(A, B, C, D) = \Sigma m(1, 5, 7, 11, 15)$$

- Since, there are four inputs A , B , C and D
- Rows of the ROM are numbered (in order) from 0 to 15.
- An X or a dot $\bullet$ is then placed at the appropriate intersection

 Example cont.

- For example, for minterm
 - 6, X 's are placed at $A'BCD'$
 - 14, X 's are placed at $ABCD'$
- To implement given functions, pass the corresponding minterms by placing dots at intersection of required minterms, giving outputs W , X and Y



Designing with Programmable Logic Arrays

- To design a system using a **PLA**, you need only find **SOP** (instead of Sum of Minterms as in case of designing with ROMs) expressions for the functions to be implemented
- The only limitation is the number of AND gates (product terms) that are available
- Any SOP expression for each of functions will be obtained by simplifying functions using K-Maps so that we can maximize sharing of gates

Example

Implement the following three functions with PLA

$$W(A, B, C, D) = \Sigma m(3, 7, 8, 9, 11, 15)$$


$$X(A, B, C, D) = \Sigma m(3, 4, 5, 7, 10, 14, 15)$$

$$Y(A, B, C, D) = \Sigma m(1, 5, 7, 11, 15)$$


- In order to implement these functions with PLA, we shall simplify them first by K-maps and then try to combine 1's such that we can maximize sharing of terms

 Example cont.

- So, K-maps for w, x and y are as follows:
- Implementation of functions with PLA is shown



 
$$\begin{aligned}
 W &= AB'C' + A'CD + ACD \\
 X &= A'BC' + A'CD + BCD + ACD' \\
 Y &= A'C'D + BCD + ACD
 \end{aligned}$$



Designing with Programmable Array Logic

- In PAL, each output comes from an OR gate that has its own group of AND gates connected to it
- Layout of a small PAL is shown
 - For this PAL, there are six inputs and four outputs, with each OR gate having four input terms
- When using PAL, output of each AND gate goes to only one OR
 - No sharing of terms, solve each function individually
 - However, most PALs provide for possible feedback of some or all of outputs to input

 

Example

Implement the following three functions with PAL.

$$W(A, B, C, D) = \Sigma m(3, 7, 8, 9, 11, 15)$$

$$X(A, B, C, D) = \Sigma m(3, 4, 5, 7, 10, 14, 15)$$

$$Y(A, B, C, D) = \Sigma m(1, 5, 7, 11, 15)$$

- In order to implement these functions with PAL, we shall simplify them first by using K-maps and then try to combine 1's such that we can minimize the functions without considering the sharing of terms
- So, K-maps for w, x and y are as follows:




Example cont.

- Implementation of the given functions with PAL (choosing first of each of optional terms) is as follows:

$$W(A, B, C, D) = \sum m(3, 7, 8, 9, 11, 15)$$

$$X(A, B, C, D) = \sum m(3, 4, 5, 7, 10, 14, 15)$$

   
$$Y(A, B, C, D) = \sum m(1, 5, 7, 11, 15)$$



$$W = AB'C' + CD$$

$$X = A'BC' + A'CD + ACD' + \{ BCD + ABC \}$$

$$Y = A'C'D + ACD + \{ A'BD + BCD \}$$

 

Example

- Implement the following three functions with PAL.




$$f(a, b, c, d) = \sum(0, 1, 5, 6, 9, 12, 14)$$

$$g(a, b, c, d) = \sum(0, 1, 5, 9, 10, 14, 15)$$

$$h(a, b, c, d) = \sum(0, 1, 2, 5, 6, 9, 10)$$

- In order to implement these functions with PAL, we shall simplify them first by using K-maps and then try to combine 1's such that we can minimize the functions without considering the sharing of terms.
- So, K-maps for f , g and h are as follows:

Example cont.

   

$$f = a'b'c' + a'c'd + b'c'd + abd' + bcd'$$

$$g = a'b'c' + a'c'd + b'c'd + abc + acd'$$

$$h = a'b'c' + a'c'd + b'c'd + a'cd' + b'cd'$$


Example cont.

- Simplified functions contain more than four terms
- Therefore, cannot be implemented with PAL
- Use feedback solution

$$f = a'b'c' + a'c'd + b'c'd + abd' + bcd'$$


$$g = a'b'c' + a'c'd + b'c'd + abc + acd'$$
 
$$h = a'b'c' + a'c'd + b'c'd + a'cd' + b'cd'$$



 Example cont.

- So, first three common terms (prime implicants) are implemented in first OR gate, output of which, t , is *fed-back* to the input of one of the AND gates in each of the other three circuits
- Note that the fourth AND gate of t circuit has both a and a' connected at its input because output of that AND gate is 0
 - Some implementations require the user to connect unused AND gates in that way
 - Not done for other unused AND gates



The End